

# 4-bit binary adder/subtractor

binary addition

$$\begin{array}{r}
 A_3 \ A_2 \ A_1 \ A_0 \\
 B_3 \ B_2 \ B_1 \ B_0 \\
 C_3 \ C_2 \ C_1 \ C_0 (=0) \\
 \hline
 C_4 \ S_3 \ S_2 \ S_1 \ S_0 \\
 \text{(Carry)}
 \end{array}$$

Ex: 
$$\begin{array}{r}
 1000 \\
 1001 \\
 \hline
 10001
 \end{array}$$

Binary Subtraction by 2's complement

$$\begin{array}{r}
 A_3 \ A_2 \ A_1 \ A_0 \\
 \bar{B}_3 \ \bar{B}_2 \ \bar{B}_1 \ \bar{B}_0 \\
 C_3 \ C_2 \ C_1 \ C_0 (=1) \\
 \hline
 \text{Carry neglected} \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}$$

Ex: Using 1's complement

$$\begin{array}{r}
 1001 \\
 - 1000 \\
 \hline
 \Rightarrow \begin{array}{r} 1001 \\ 0111 \\ \hline 10000 \\ +1 \\ \hline 0001 \text{ result} \end{array}
 \end{array}$$

positive

$$\begin{array}{r}
 1000 \\
 - 1001 \\
 \hline
 \Rightarrow \begin{array}{r} 1000 \\ 0110 \\ \hline 01110 \\ \hline 0001 \\ \text{result is 1's complement} \end{array}
 \end{array}$$

negative

Using 2's complement

$$\begin{array}{r}
 1001 \\
 - 1000 \\
 \hline
 \end{array}$$

2's complement of 1000 = 
$$\begin{array}{r}
 0111 \\
 +1 \\
 \hline
 1000
 \end{array}$$

$$\begin{array}{r}
 1001 \\
 + 1000 \\
 \hline
 10001 \rightarrow \text{result} \\
 \text{positive \& neglect}
 \end{array}$$


$$\begin{array}{r}
 1000 \\
 - 1001 \\
 \hline
 \end{array}$$

2's complement of 1001 = 
$$\begin{array}{r}
 0110 \\
 +1 \\
 \hline
 0111
 \end{array}$$

$$\begin{array}{r}
 1000 \\
 + 0111 \\
 \hline
 1111
 \end{array}$$

$\rightarrow$  Negative  
 Result is 2's complement of 1111  
 $= (-) 0001$

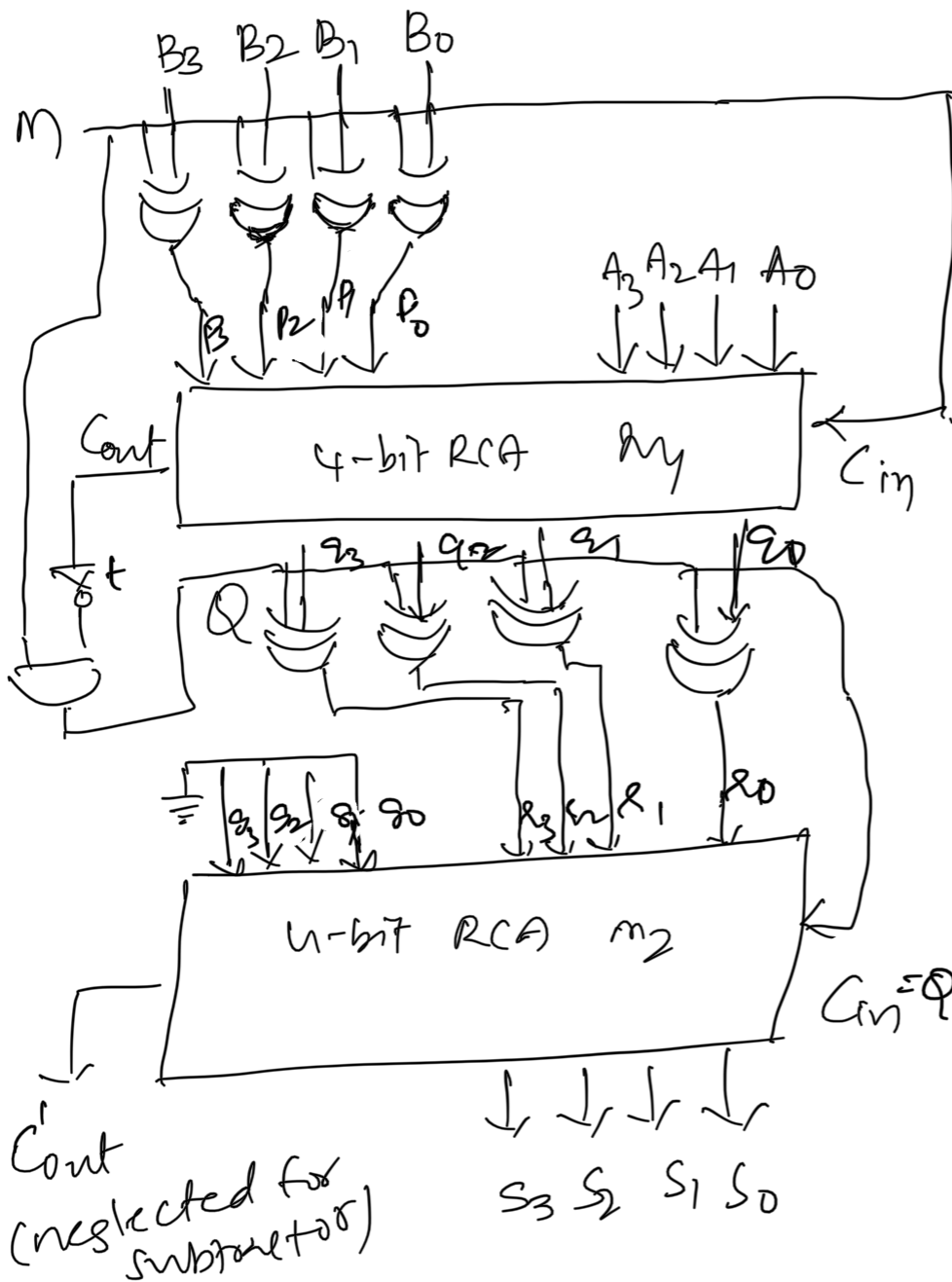Now we implement common circuit for 4-bit binary adder & subtractor.



$m=0$  addition  
 $m=1$  subtraction

$A_3 A_2 A_1 A_0$  is  
 common for all

if  $m=0$ , XOR gate sends  $B_3 B_2 B_1 B_0$   
 if  $m=1$ , XOR gate sends  $\bar{B}_3 \bar{B}_2 \bar{B}_1 \bar{B}_0$  (1's complement)  
 but we want 2's complement so  $C_{in} = m (=0/1)$

M	cout	Q
0	0	0
0	1	0
1	0	1
1	1	0

$$Q = m \bar{C}_{out}$$

Consider for addition